
## COUNTER CIRCUIT

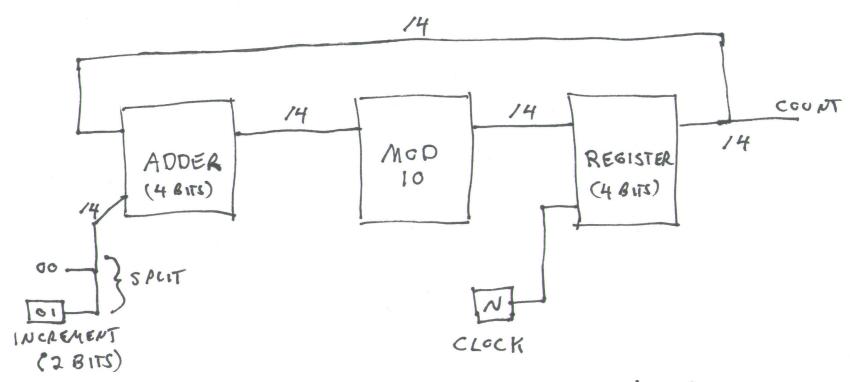

14 -7 NEED 4 BITS TO COUNT & TO 9